




Section 2B1

**NAME** .....**ID**

**DAMISU SEFU** ..... **UGR/5286/12**

**DATE OF SUBMISSION**      **AUG 24/2021**

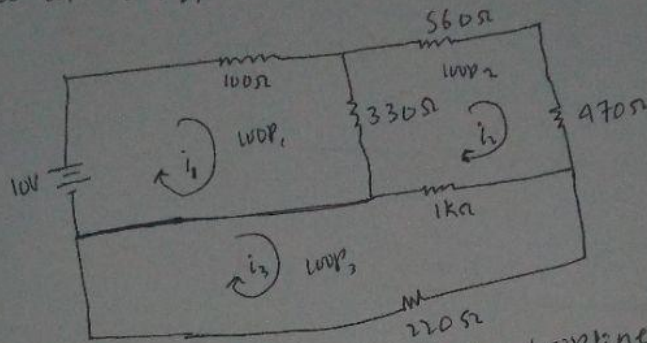2.1 For the circuit of the Figure-10 find the current in each element and voltage across each element. Show Kirchhoff's law are satisfied.



By applying mesh analysis for loopline  
for mesh 1 (loop 1) KVL

$$-10V + 100i_1 + 330(i_1 - i_2) = 0$$

$$430i_1 - 330i_2 = 10V \text{ ----- equation (*)}$$

for mesh 2 (loop 2) KVL

$$560i_2 + 470i_2 + 330(i_2 - i_1) + 1000(i_2 - i_3) = 0$$

$$2360i_2 - 330i_1 - 1000i_3 = 0 \text{ ----- equation (**)}$$

for mesh 3 (loop 3) KVL

$$220i_3 + 1000(i_3 - i_2) = 0$$

$$1220i_3 - 1000i_2 = 0 \text{ ----- equation (***)}$$

by solving the above three system of equation.

$$1220i_3 - 1000i_2 = 0$$

$$2360i_2 - 330i_1 - 1000i_3 = 0$$

$$2.8792 \times 10^6 i_2 - 4.02 \times 10^5 i_1 - 1 \times 10^6 i_3 = 0$$

$$1.8792 \times 10^6 i_2 - 4.02 \times 10^5 i_1 = 0$$


$$930i_2 - 330i_1 = 10V$$

$$i_1 = 27.84 \text{ mA}$$

$$i_2 = 5.99 \text{ mA}$$

$$i_3 = 4.9 \text{ mA}$$



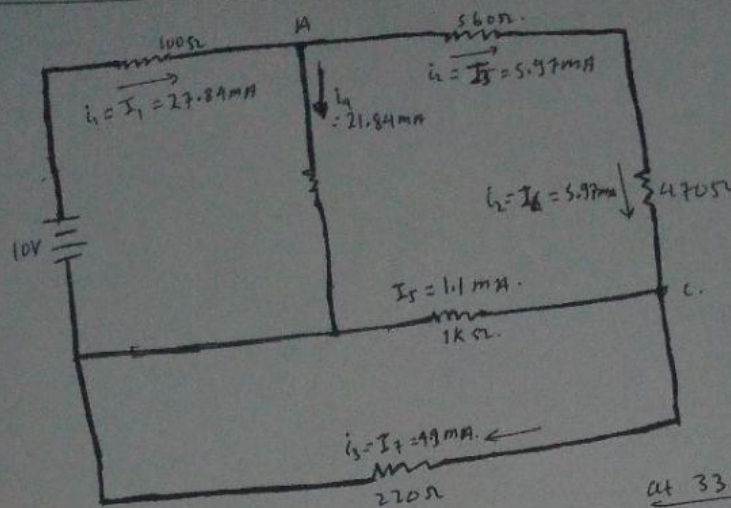

at node A  
 $I_A = i_1 - i_2 = 21.87 \text{ mA}$   
 KCL at node C  
 $I_5 = i_2 - i_1 = 1.1 \text{ mA}$   
 $I_3 = i_2 = 5.97 \text{ mA}$   
 $I_1 = i_1 = 27.84 \text{ mA}$   
 $I_6 = i_2 = 5.97 \text{ mA}$   
 $I_7 = i_3 = 4.9 \text{ mA}$

The Voltage drop at

100Ω Resistor  $V_1 = i_1 R_1 = 27.84 \times 100$   
 $V_1 = 2.78 \text{ V}$

at 560Ω Resistor  $V_2 = i_2 R_2 = 5.97 \text{ mA} \times 560 \Omega$   
 $= 3.34 \text{ V}$

at 220Ω  $V_3 = i_3 R_3 = 4.9 \text{ mA} \times 220 \Omega$   
 $= 1.1 \text{ V}$

at 330Ω Resistor  $V_4 = I_5 \times R_4$   
 $V_4 = 1.1 \text{ mA} \times 330 \Omega$   
 $= 0.363 \text{ V}$

at 1kΩ Resistor  $V_5 = I_5 R_5$   
 $V_5 = 1.1 \text{ mA} \times 1000 \Omega$   
 $V_5 = 1.1 \text{ V}$

~~at 220Ω~~  
 let's check for the Kirchhoff's law

KCL at node A i.e.

$i_1 = i_2 + I_4$   
 $27.84 \text{ mA} = 21.87 \text{ mA} + 5.97 \text{ mA}$   
 $27.84 \text{ mA} \approx 27.84 \text{ mA}$

KCL at node C

$i_2 = I_5 + I_3 = 5.97 \text{ mA} = 5.97 \text{ mA}$

KVL at each mesh is also satisfied


KVL mesh 1  $-10 \text{ V} + 2.78 \text{ V} + 3.34 \text{ V} = 0$

KVL at mesh 2


$-2.78 \text{ V} + 2.81 \text{ V} + 1.1 \text{ V} + 3.34 \text{ V} = 0$

KVL at mesh 3


$1.1 \text{ V} - 1.1 \text{ V} = 0$

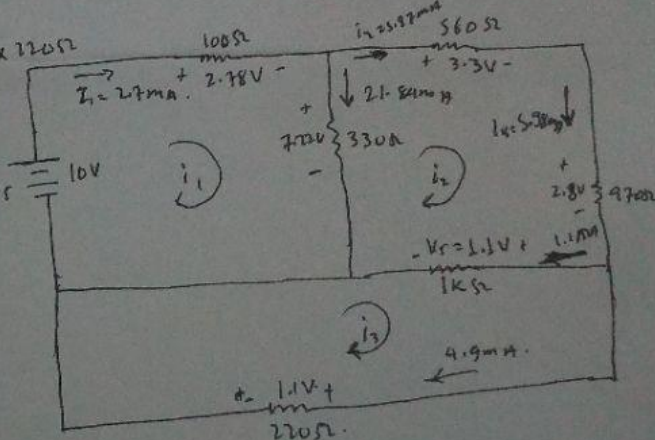

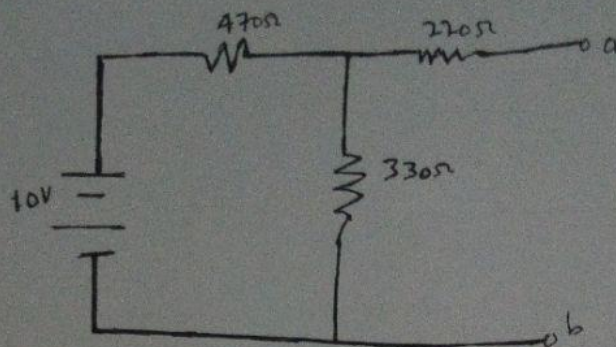2.2: For the circuit of figure-11, find the Thevenin's equivalent circuit across terminals a-b.



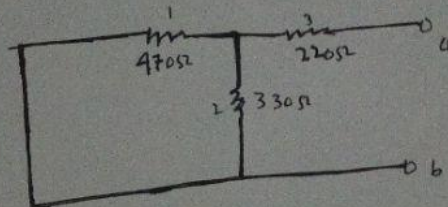
Let us find  $R_{Th}$  to find  $R_{Th}$  we could turnoff the voltage source.



Resistor  $470\Omega$  and  $330\Omega$  are in parallel so we can find their equivalent resistor by

$$R_{12} = \frac{R_1 \times R_2}{R_1 + R_2} = \frac{330\Omega \times 470\Omega}{330\Omega + 470\Omega}$$
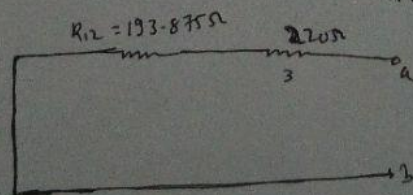
$$R_{12} = \frac{155100\Omega}{800\Omega} = 193.875\Omega$$




Now  $R_{12}$  and  $R_3$  are in series we can find their equivalent resistor by  $R_{123} = R_{12} + R_3$

$$R_{123} = 193.875\Omega + 220\Omega = 413.875\Omega$$

Since  $R_{Th} = R_{a-b} = R_{123} \Rightarrow R_{Th} = 413.875\Omega$



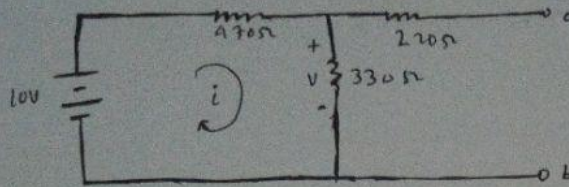Let us find the Thevenin's Voltage . to find  $V_{Th}$ .  
 we can use mesh analysis.



The Resistor  $220\Omega$  is not transfer current or the current is not pass through because at terminal a and b there is no closed system.


Therefore the only terminal Resistor which carry current is the  $330\Omega$  Resistor.

$$-10V + 470\Omega i + 330\Omega i = 0$$


$$800\Omega i = 10V$$

$$i = \underline{\underline{\frac{1}{80} A}}}$$
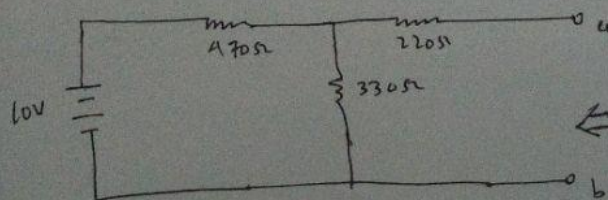
$$V_{Th} = (330\Omega) \left( \frac{1}{80} A \right) = \underline{\underline{4.125 V}}$$



become  
 Thevenin's  
 equivalent.

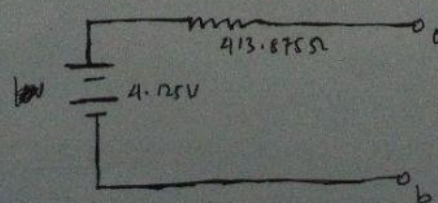

THANK  
YOU!!